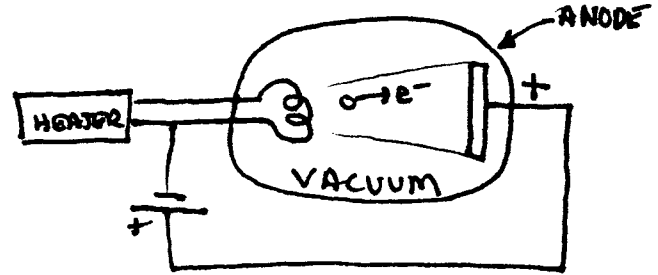


- ③ Consider the diagram to the right of a very secret thing known only as THE DEVICE. (a) What is the direction of the current in the vacuum? (b) electrons hit the anode at rate of  $6.0 \times 10^{12}/s$ . What is the current in THE DEVICE?



(a) CURRENT flows in the direction of POSITIVE CHARGE, so from ANODE TO FILAMENT.

(b) The current is the charge per unit time, defined for the direction POSITIVE CHARGES FLOW. A flow of electrons in one direction is the NEGATIVE of the current:

$$I = \text{current} = \text{RATE} * |Q_{\text{electron}}| = \underbrace{\frac{N_{\text{electron}}}{\text{time}}}_{\text{RATE}} * |Q_{\text{electron}}|$$

$$\text{so // } I = \frac{6.0 \times 10^{12}}{1s} \cdot 1.60 \times 10^{-19} C$$

$$\boxed{I = 9.6 \times 10^{-7} \text{ Amps}} \quad (\text{ANS})$$

- ⑪ The starter motor on an AuroBOT draws 220.0 A of current from a 12.0 V battery for 1.20 s. (a) How much charge is pumped by the battery? (b) How much electrical energy is supplied by the battery?



- (a) I can get charge from the definition of current:

$$I = \frac{\Delta Q}{\Delta t} \Rightarrow \Delta Q = I \Delta t = (220.0 \text{ A})(1.20 \text{ s}) = \boxed{264 \text{ C}} \quad \begin{array}{l} \text{LOTS} \\ \text{OF} \\ \text{CHARGE!} \\ \text{(ANS)} \end{array}$$

- (b) I choose a particular form to express Power based on WHAT I KNOW. In this case, I know VOLTAGE and CURRENT so:  $P = IV$  seems useful. To get energy I appeal to the definition of power:

$$P = \frac{\Delta E}{\Delta t} \rightarrow \Delta E = P \Delta t = IV \Delta t \\ = (220.0 \text{ A})(12.0 \text{ V})(1.20 \text{ s})$$

$$\boxed{\Delta E = 3170 \text{ J}} \quad \text{(ANS)}$$

- ⑫ A SOLAR CELL provides an EMF of 0.45 V. (a) If the cell yields a constant 18.0 mA current for 9.0 h, how much electrical energy does it supply? (b) What is the rate it supplies energy (the power)?
- 

(a) Since I know VOLTAGE (EMF) and current,  $P = IV$  is good for computing power. I can get energy from power:


$$P = \frac{\Delta E}{\Delta t} \Rightarrow \Delta E = P \Delta t = IV \Delta t \\ = (18.0 \times 10^{-3} \text{ A})(0.45 \text{ V})(32400 \text{ s})$$

$$\boxed{\Delta E = 262 \text{ J}} \quad (\text{ANS})$$

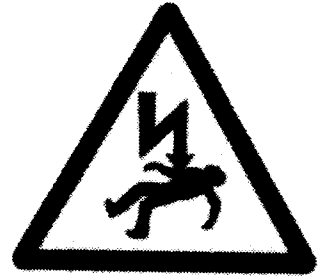(b) As noted above, I can get power from:

$$P = IV = (18.0 \times 10^{-3} \text{ A})(0.45 \text{ V}) = \boxed{8.1 \times 10^{-3} \text{ W}} \quad (\text{ANS})$$

- ② A current as small as 50 mA near your heart can kill you. Suppose a nervous electrician has  $R = 1\text{ k}\Omega$  from hand to hand and touches two wires. (a) What potential difference between the two wires will generate a 50 mA current between hands? (b) When working on a live circuit, keep one hand behind your back — why?




- (a) Touching the two wires makes a circuit, with our heroic electrician playing the role of resistor. Applying Ohm's Law gives us the Voltage between the wires:

$$V = IR = (50 \times 10^{-3} \text{ A})(1000 \Omega) = \boxed{50 \text{ V}} \text{ (ANS)}$$

Note in the US the most common voltage is 120 V, much higher than this.

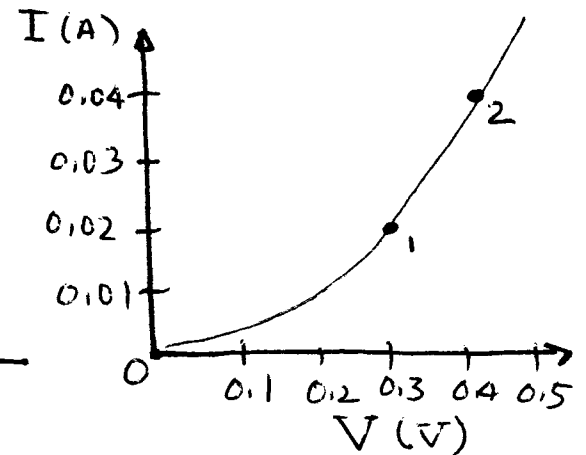- (b) By keeping one hand behind your back, you will never (at least not easily) close a circuit using the path thru your heart as a resistor.

- ②6 A TOP SECRET DEVICE has an  $I$  vs  $V$  graph shown at right. What is resistance at points 1 and 2?




The material is not perfectly ohmic because the graph is not linear over the entire range. HOWEVER, between pts 1 and 2, it IS approximately linear (OHMIC) with slope

$$\text{SLOPE} = \frac{\Delta I}{\Delta V} = \frac{0.02 \text{ A}}{0.1 \text{ V}} = 0.2 \frac{\text{A}}{\text{V}}$$

The inverse of this slope is the resistance in this linear regime by Ohm's Law. Since 1 and 2 are in the same region of the graph (connected by a STRAIGHT LINE) they have the same  $R$ :

$$V = IR \Rightarrow R = \frac{V}{I} = \frac{1}{\text{SLOPE}} = \boxed{5 \Omega} \quad (\text{ANS})$$

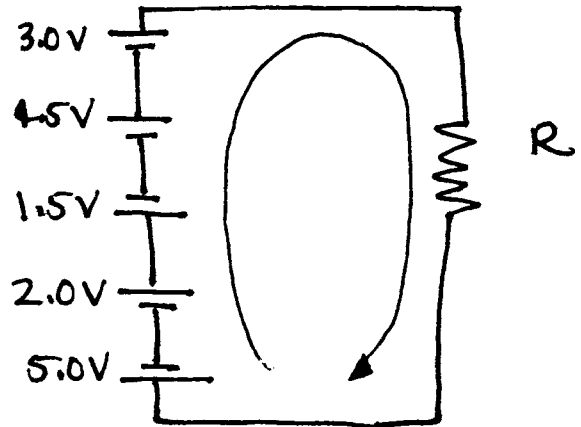- 36) When I crash on a desert island, I have a handful of mismatched batteries to power my GAMEBOY (R).  
 (a) Hooked up as shown, what EMF is provided?  
 (b) What is the current thru my Gameboy if it has  $R = 3.2 \Omega$ ?



- a) Suppose the current flows in the direction indicated by the arrow in the loop. EMF oriented with this arrow contribute positively, those oriented against contribute negatively. So:


$$\mathcal{E}_{TOT} = 3.0V + 4.5V - 1.5V + 2.0V - 5.0V = \boxed{3.0V} \quad (\text{ANS})$$

EXACTLY THE VOLTAGE REQUIRED  
BY MY GAMEBOY!

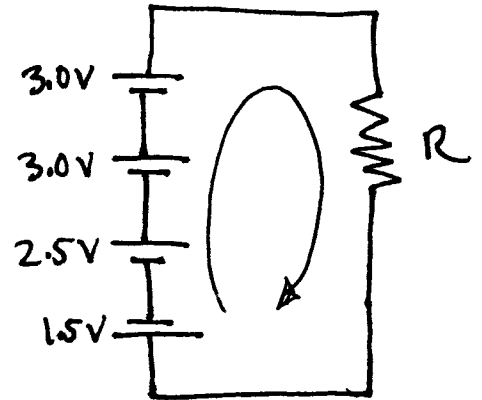- (b) I can get the current using Ohm's Law with the TOTAL EMF:

$$V = IR \Rightarrow I = \frac{V}{R} = \frac{\mathcal{E}_{TOT}}{R} = \frac{3.0V}{3.2\Omega} = \boxed{0.94 \text{ Amps}} \quad (\text{ANS})$$

- ② I also find on my desert island a satellite phone. I grudgingly give up some Gameboy batteries to see if it will work as shown here. (a) What is my total EMF? (b) If I output 0.40 A, what is the resistance  $R$  of my satellite phone?




- (a) As in the previous problem, I assume the current flows in the direction of the arrow, so:

$$\mathcal{E}_{\text{TOT}} = 3.0\text{V} + 3.0\text{V} + 2.5\text{V} - 1.5\text{V} = \boxed{7.0\text{V}} \quad (\text{ANS})$$

- (b) I can get  $R$  from Ohm's Law and  $\mathcal{E}_{\text{TOT}}$ :

$$V = IR \rightarrow R = \frac{V}{I} = \frac{\mathcal{E}_{\text{TOT}}}{I} = \frac{7.0\text{V}}{0.40\text{A}} = \boxed{17.5\Omega} \quad (\text{ANS})$$

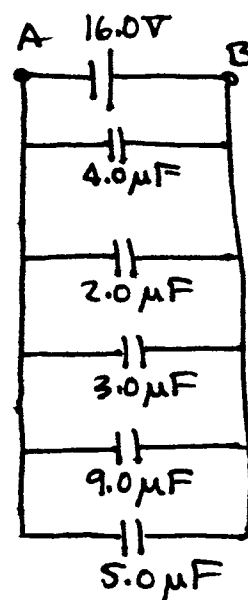
- 39) Having failed to power my satellite phone in 37) I resort to building capacitor networks out of coconuts, like the one shown here. (a) What is the equivalent capacitance for this network? (b) What is the charge on a single  $C_{eq}$  that could replace this network? (c) What is the charge on the  $3.0\mu\text{F}$  capacitor?



- (a) All the capacitors are in PARALLEL. In this case, the  $C_{eq}$  is:

$$\begin{aligned} C_{eq} &= C_1 + C_2 + C_3 + C_4 + C_5 \\ &= 4.0\mu\text{F} + 2.0\mu\text{F} + 3.0\mu\text{F} + 9.0\mu\text{F} + 5.0\mu\text{F} \\ &= \boxed{23.0\mu\text{F}} \quad (\text{ANS}) \end{aligned}$$

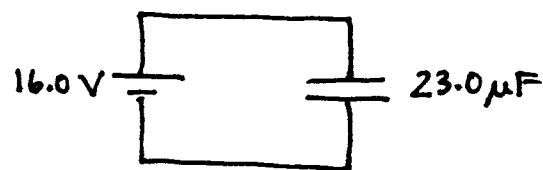- (b) The equivalent circuit seen by the battery is at right. The voltage that charges the capacitor is the 16.0V battery, so the  $Q_{eq}$  is:




$$\begin{aligned} C_{eq} &= \frac{Q_{eq}}{V} \Rightarrow Q_{eq} = V C_{eq} = \mathcal{E} C_{eq} = 16.0\text{V} \cdot 23 \times 10^{-6}\text{F} \\ &= \boxed{3.7 \times 10^{-4}\text{C}} \quad (\text{ANS}) \end{aligned}$$


- (c) Since EVERY capacitor is in parallel, they have the same  $V = \mathcal{E} = 16\text{V}$  across them. So for the  $3.0\mu\text{F}$  capacitor:

$$C = \frac{Q}{V} \Rightarrow Q = C V = C \mathcal{E} = (3.0 \times 10^{-6}\text{F})(16\text{V}) = \boxed{4.8 \times 10^{-5}\text{C}} \quad (\text{ANS})$$

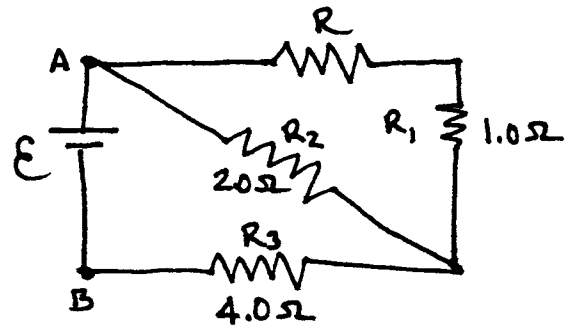- (42) In my quest to design a better FLUX CAPACITOR, one of my brilliant students suggests this circuit might be useful. The applied emf is  $\mathcal{E} = 93.5 \text{ V}$ , and the current thru  $R_3$  is  $17 \text{ A}$ . How big is  $R$ ?




For complex looking circuits like this, I can redraw them in a more conventional form to make it easier to understand what is going on. I can move ANY WIRE so long as it does not cross another circuit element (junction, battery, resistor, wire, etc). I can check my redrawn circuit by checking that along any given loop I encounter the same elements in both diagrams. Keeping this in mind, the crazy circuit above may be redrawn as:

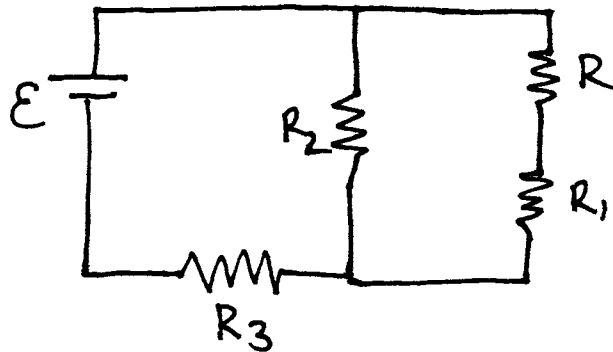


There are a variety of ways to solve for  $R$ . The following is the most straight forward. I begin by working out all my reduced circuits to get the battery view.

REDUCTION 1: R in SERIES with  $R_1$

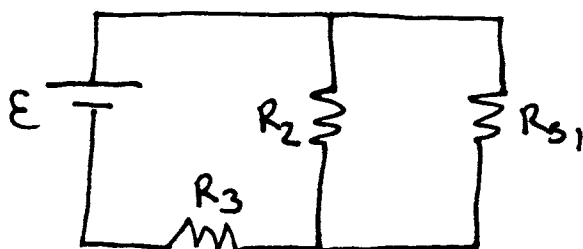

$$R_{S1} = R + R_1$$

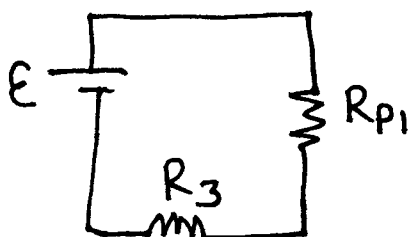REDUCTION 2:  $R_2$  in PARALLEL with  $R_{S1}$



$$\frac{1}{R_{P1}} = \frac{1}{R_{S1}} + \frac{1}{R_2} = \frac{1}{R+R_1} + \frac{1}{R_2}$$


↓ COMMON DENOMINATOR

$$\frac{1}{R_{P1}} = \frac{R_2}{R_2(R+R_1)} + \frac{R+R_1}{R_2(R+R_1)}$$

$$= \frac{R+R_1+R_2}{R_2(R+R_1)}$$

$$\Rightarrow R_{P1} = R_2(R+R_1) / (R+R_1+R_2)$$

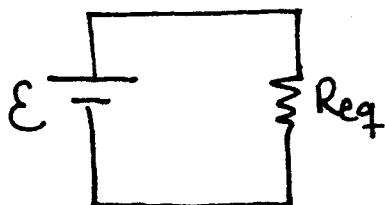REDUCTION 3:  $R_{P1}$  in SERIES with  $R_3$



$$R_{eq} = R_3 + R_{P1}$$

$$R_{eq} = R_3 + \frac{R_2(R+R_1)}{R+R_1+R_2}$$

If I knew the numerical value of  $R_{eq}$  then I know all resistance except  $R$ , and could find  $R$  from the  $R_{eq}$  result.



I can find  $R_{eq}$  from the given voltage and current. The 17A current thru  $R_3$  (4 $\Omega$  resistor) is the SAME current that goes thru the battery — current is not used up ever, and there are no junctions between  $R_3$  and the battery. SO 17A must be the current that flows around the circuit in REVOLUTION 3 above.

Use Ohm's law to find  $R_{eq}$ :

$$V = IR \rightarrow R = \frac{V}{I} \rightarrow R_{eq} = \frac{E}{I} = \frac{93.5V}{17A} = 5.5\Omega$$

So the Resistance are:  $R_{eq} = 5.5\Omega$        $R_2 = 2.0\Omega$   
 $R_1 = 1.0\Omega$        $R_3 = 4.0\Omega$

and/

$$R_{eq} = R_3 + \frac{R_2(R+R_1)}{R+R_1+R_2} \rightarrow 5.5\Omega = 4.0\Omega + \frac{2.0\Omega(R+1.0\Omega)}{R+1.0\Omega+2.0\Omega}$$

$$\rightarrow 5.5\Omega - 4.0\Omega = \frac{R \cdot (2.0\Omega) + 2.0\Omega^2}{R + 3.0\Omega}$$


$$\rightarrow 1.5\Omega = \frac{R(2\Omega) + 2\Omega^2}{R + 3\Omega} \rightarrow 1.5\Omega(R+3\Omega) = R(2\Omega) + 2\Omega^2$$

$$\rightarrow R(1.5\Omega) + 4.5\Omega^2 = R(2\Omega) + 2\Omega^2$$

$$\rightarrow R(2\Omega) - R(1.5\Omega) = 4.5\Omega^2 - 2\Omega^2$$


$$\rightarrow R(0.5\Omega) = 2.5\Omega^2 \rightarrow R = \frac{2.5\Omega^2}{0.5\Omega} = \boxed{5\Omega = R} \text{ (ANS)}$$

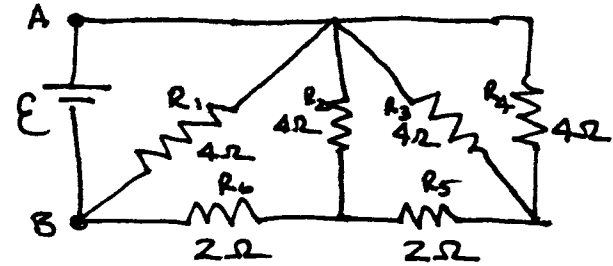⑤) After the last circuit blew up we replaced it with this new improved crazy circuit.



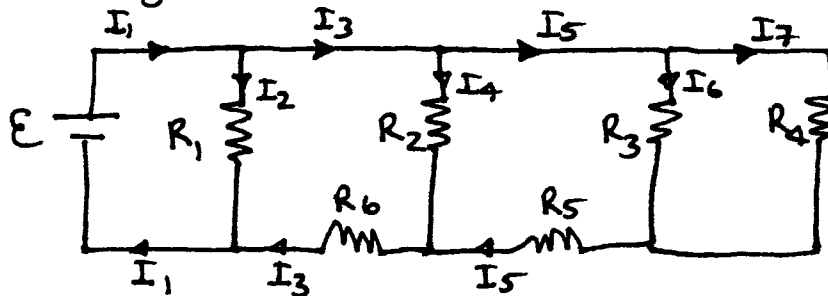(a) What is the equivalent resistance of this network? (b) What current flows thru the battery ( $\mathcal{E} = 6.0\text{V}$ )? (c) What current flows thru  $R_4$  ( $R_4 = 4.0\Omega$ )?

First step is to draw a standardized diagram by sliding wire contacts around. I get:



Now I reduce this (to give me part a):


REDUCTION 1:  $R_3$  in PARALLEL with  $R_4$



$$\begin{aligned}\frac{1}{R_{p1}} &= \frac{1}{R_3} + \frac{1}{R_4} \\ &= \frac{1}{4\Omega} + \frac{1}{4\Omega} = \frac{2}{4\Omega}\end{aligned}$$

$$\text{so } R_{p1} = 2\Omega$$

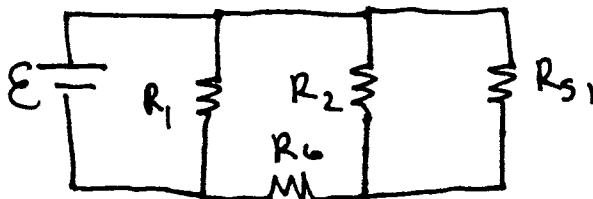REDUCTION 2:  $R_5$  in SERIES with  $R_{p1}$



$$\begin{aligned}R_{s1} &= R_5 + R_{p1} \\ &= 2\Omega + 2\Omega\end{aligned}$$

$$R_{s1} = 4\Omega$$


REDUCTION 3:  $R_2$  in PARALLEL with  $R_{S1}$



$$\frac{1}{R_{P2}} = \frac{1}{R_2} + \frac{1}{R_{S1}} = \frac{1}{4\Omega} + \frac{1}{4\Omega} = \frac{2}{4\Omega}$$

$$\boxed{R_{P2} = 2\Omega}$$

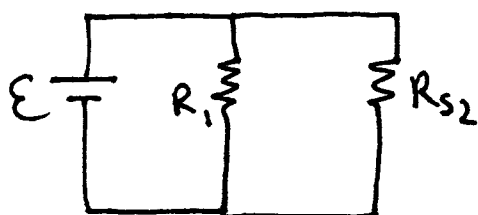REDUCTION 4:  $R_6$  in SERIES with  $R_{P2}$



$$\begin{aligned} R_{S2} &= R_{P2} + R_6 \\ &= 2\Omega + 2\Omega \end{aligned}$$

$$\boxed{R_{S2} = 4\Omega}$$

REDUCTIONS:  $R_1$  in PARALLEL with  $R_{S2}$



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_{S2}} = \frac{1}{4\Omega} + \frac{1}{4\Omega} = \frac{2}{4\Omega}$$

$$\text{or, } \boxed{R_{eq} = 2\Omega} \quad (\text{ANS})$$

(b) I can get the current that flows thru the battery from Ohm's Law and my last reduction, that shows me how the circuit looks to the battery

$$V = IR \rightarrow I = \frac{V}{R} = \frac{\mathcal{E}}{R_{eq}} = \frac{6.0\text{V}}{2\Omega} = \boxed{3.0\text{Amps}} \quad (\text{ANS})$$




(c) Since I want to know the current in  $R_4$ , I need to figure out how the current divides at each junction between the battery (where I know the current) and  $R_4$ . There are 7 different currents in the circuit (as labeled in my standardized diagram).

To find the currents I use the LOOP RULE and JUNCTION RULE.

STEP 1:  $I_2$  &  $I_3$

LOOP  
RULE

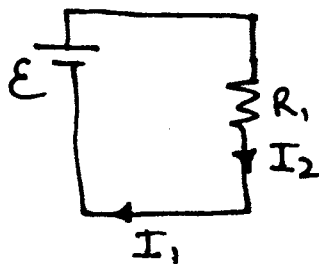

$$\mathcal{E} - V_1 = 0$$

$$\mathcal{E} = V_1 = R_1 \cdot I_2$$

$$\text{so// } I_2 = \frac{\mathcal{E}}{R_1} = \frac{6.0\text{V}}{4\Omega} = 1.5\text{A}$$


JUNCTION  
RULE :  $I_1 = I_2 + I_3$

$$\text{so// } I_3 = I_1 - I_2 = 3.0\text{A} - 1.5\text{A} = 1.5\text{A}$$

$$\text{so// } \boxed{\begin{array}{l} I_2 = 1.5\text{A} \\ I_3 = 1.5\text{A} \end{array}}$$

STEP 2:  $I_4$  and  $I_5$

LOOP  
RULE

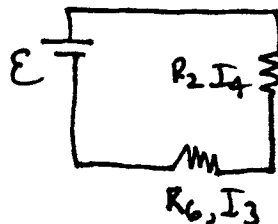

$$\mathcal{E} - V_2 - V_6 = 0$$

$$\mathcal{E} - R_2 \cdot I_4 - R_6 \cdot I_3 = 0$$


$$R_2 \cdot I_4 = \mathcal{E} - R_6 \cdot I_3$$

$$\text{or// } I_4 = \frac{\mathcal{E} - R_6 \cdot I_3}{R_2} = \frac{6\text{V} - 22 \cdot 1.5\text{A}}{4\Omega} = 0.75\text{A}$$

JUNCTION  
RULE :  $I_3 = I_4 + I_5$

$$\text{so// } I_5 = I_3 - I_4 = 1.5\text{A} - 0.75\text{A} = 0.75\text{A}$$

$$\text{so// } \boxed{\begin{array}{l} I_4 = 0.75\text{A} \\ I_5 = 0.75\text{A} \end{array}}$$

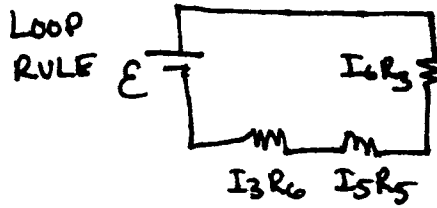STEP 3:  $I_6$  and  $I_7$ 

$$\mathcal{E} - V_3 - V_5 - V_6 = 0$$

$$\mathcal{E} - I_6 R_3 - I_5 R_5 - I_3 R_6 = 0$$

$$I_6 R_3 = \mathcal{E} - I_5 R_5 - I_3 R_6$$

$$\text{or} // I_6 = \frac{\mathcal{E} - I_5 R_5 - I_3 R_6}{R_3}$$

$$= \frac{6.0 \text{ V} - 0.75 \text{ A} \cdot 2 \Omega - 1.5 \text{ A} \cdot 2 \Omega}{4 \Omega}$$


$$= \frac{1.5 \text{ V}}{4 \Omega} = 0.375 \text{ A}$$

JUNCTION RULE:  $I_5 = I_6 + I_7$


$$I_7 = I_5 - I_6 = 0.75 \text{ A} - 0.375 \text{ A} = 0.375 \text{ A} = I_7$$

(ANS)

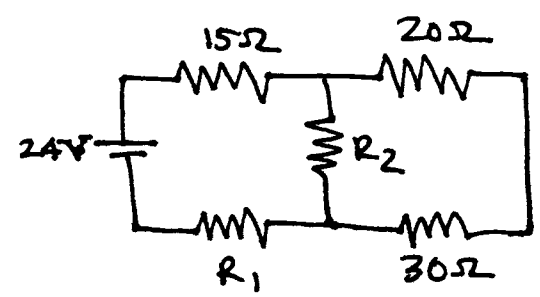⑥7 For some reason that is unclear to me, I gave you this perfectly ordinary looking circuit to analyze.  $\therefore$  Take  $R_1 = 10\Omega$  and  $R_2 = 15\Omega$ . (a) What is  $R_{eq}$  for the circuit? (b) What current flows thru  $R_1$ ? (c) What is Voltage drop across  $R_2$ ? (d) What current flows thru  $R_2$ ? (e) How much power is dissipated in  $R_2$ ?




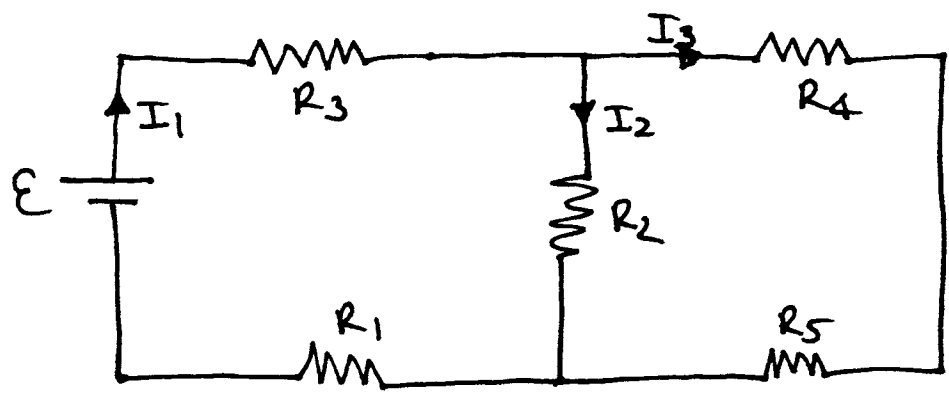So this is extremely similar to the last 2 problems, and I'll follow a similar strategy. Let me redraw the circuit with labels instead of numbers:



- $R_1 = 10\Omega$
- $R_2 = 15\Omega$
- $R_3 = 15\Omega$
- $R_4 = 20\Omega$
- $R_5 = 30\Omega$
- $E = 24V$

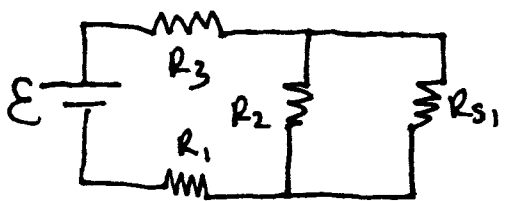
REDUCTION 1:  $R_4$  in SERIES with  $R_5$



$$R_{s1} = R_4 + R_5 = 20\Omega + 30\Omega = 50\Omega$$



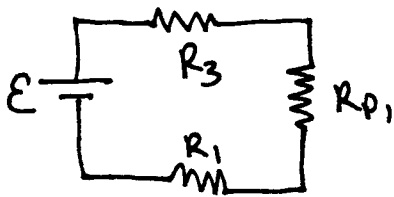
REDUCTION 2:  $R_2$  in PARALLEL with  $R_{S1}$



$$\frac{1}{R_{P1}} = \frac{1}{R_2} + \frac{1}{R_{S1}} = \frac{R_{S1} + R_2}{R_2 \cdot R_{S1}}$$

$$R_{P1} = \frac{R_2 \cdot R_{S1}}{R_2 + R_{S1}} = \frac{(15\Omega)(50\Omega)}{15\Omega + 50\Omega} = 11.5\Omega$$

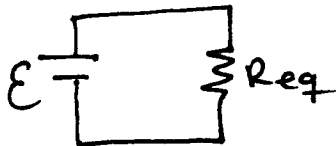REDUCTION 3:  $R_3$  in SERIES with  $R_{P1}$  in SERIES with  $R_1$




$$\begin{aligned} R_{eq} &= R_3 + R_{P1} + R_1 \\ &= 15\Omega + 11.5\Omega + 10\Omega \end{aligned}$$

$$\boxed{R_{eq} = 36.5\Omega} \quad (\text{ANS})$$

(b) The current through  $R_1$  is the same as the current thru the battery ( $I_1$ ), which I can find from Ohm's Law and  $R_{eq}$ :

$$V = IR \Rightarrow I = \frac{V}{R} = \frac{\mathcal{E}}{R_{eq}} = \frac{24.0\text{V}}{36.5\Omega} = \boxed{0.658\text{A} = I_1} \quad (\text{ANS})$$

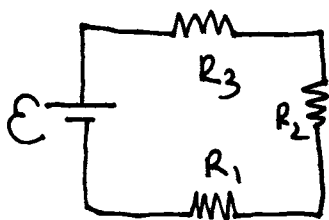(c) To get voltage  $V_2$  across  $R_2$  I use the LOOP RULE: the current thru  $R_1$  and  $R_3$  is  $I_1$ , thus:



$$\mathcal{E} - V_3 - V_2 - V_1 = 0$$

$$\mathcal{E} - I_1 R_3 - V_2 - I_1 R_1 = 0$$

$$\text{or } V_2 = -I_1(R_1 + R_3) + \mathcal{E} = -0.658\text{A}(25\Omega) + 24\text{V}$$

$$\boxed{V_2 = 7.55\text{V}} \quad (\text{ANS}) \quad \rightarrow$$


(d) If I know the voltage drop, I can find the current from Ohm's Law:

$$V = IR \rightarrow I = \frac{V_2}{R_2} = \frac{7.55V}{15\Omega} = \boxed{0.50A = I_2} \quad (\text{ANS})$$

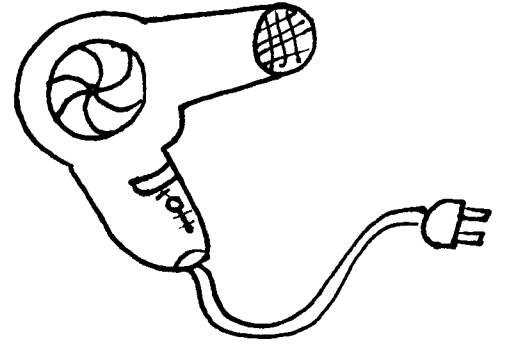(e) Power dissipated may be computed in several ways.  
A convenient way is:

$$P = IV = \underbrace{(0.50A)}_{I_2} \cdot \underbrace{(7.55V)}_{V_2} = \boxed{3.78W = P_2} \quad (\text{ANS})$$

- 103 (a) What is the resistance of a 1500W dryer that plugs into a 120V outlet? (b) What current does the hair dryer draw when turned on? (c) How much does it cost to run the hair dryer for 5.00m at \$0.10/kW·h? (d) In a 240V outlet in Europe, how much power is the dryer using? (e) What current does it draw from 240V?



(a) I can find resistance from the definition of power:

$$P = \frac{V^2}{R} \rightarrow R = \frac{V^2}{P} = \frac{(120V)^2}{1500W} = \boxed{9.6\Omega = R} \quad (\text{ANS})$$

(b) I can find the current from another definition of power:

$$P = IV \rightarrow I = \frac{P}{V} = \frac{1500W}{120V} = \boxed{12.5A_{mp} = I} \quad (\text{ANS})$$

(c) The cost is:  $C = \text{PRICE} * \text{POWER} * \text{TIME}$

$$\text{sol} \quad C = \left(\frac{\$0.10}{\text{kW}\cdot\text{h}}\right) \left(\frac{1\text{h}}{3600\text{s}}\right) \left(\frac{1\text{kW}}{1000\text{W}}\right) \cdot 1500\text{W} \cdot 5\text{m} \left(\frac{60\text{s}}{1\text{m}}\right)$$

$$\boxed{C = \$0.0125 = 1\text{cent}} \quad (\text{ANS})$$

(d) The physical properties of the hair dryer are fixed, notably the resistance  $R$ , which controls the current that flows for a given applied voltage. The power then is:

$$P = \frac{V^2}{R} = (240\text{V})^2 / 9.6\Omega = \boxed{6000\text{W}} \quad \text{! HUGE!} \quad (\text{ANS})$$

(e) By a similar argument as in d, the current drawn is affected by the resistance and applied voltage  
so //

$$V = IR \Rightarrow I = \frac{V}{R} = \frac{240\text{V}}{9.6\Omega} = \boxed{25\text{AMPS}} \quad (\text{ANS})$$